


Q.P. Code : 731401

(3 Hours)

[Total Marks : 80

- N.B. :** (1) Question number one is **compulsory** and from the rest of the questions solve any **three**.
(2) Assume suitable data wherever required.

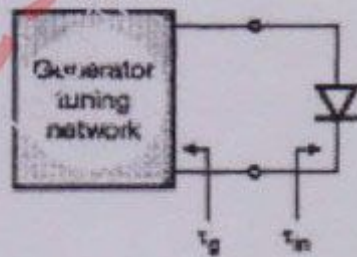1. (a) Explain the criteria for substrate material selection in MMIC. 20
(b) How the coupled line parameters varies with frequency ?
(c) What is optimum termination for an Microwave Amplifier ?
(d) Explain Dielectric resonator oscillator in detail.
2. (a) Determine the stability of GaAs FET that has the following S-parameters 10
at 2 GHz in 50Ω system both graphically and mathematically.
 $S_{11} = 0.86 \angle -57^\circ$, $S_{21} = 3 \angle 125^\circ$
 $S_{12} = 0.018 \angle 61.5^\circ$, $S_{22} = 0.775 \angle -26^\circ$
(b) Derive an Expression for Transducer Power Gain of an Amplifier. 10
3. (a) Design one port oscillator using tunnel diode with $\tau_{in} = 1.25 \angle 40^\circ$ at 8 10
GHz in 50Ω system



- (b) Explain Dielectric resonator oscillator in detail 10
4. (a) Explain two Coupled Line operated as four port microwave device. 5
(b) What is Planar Waveguide. Describe its parameters. 10
(c) Describe any fabrication process for the MMIC. 5

5. (a) Discuss Various Mixer Topologies and Compare their performances. 10
- (b) What are the causes of low frequency noise and high frequency noise associated with the mixer? 5
- (c) Explain Large signal characterization with reference to load pull counters, how it is measured? 5
6. Write short note 20
- (a) Compressed Smith Chart
 - (b) Double Balanced Mixer
 - (c) Micro strip Line for Millimetre wave
 - (d) Amplifier Linearization Methods
-