

Sem-III (Comp)

18105116

Electronic Circuits & Comm. Fundamentals
(CBGS & Revised)

QP Code : 30607

Time:-3 Hrs

Marks: 80

N.B. : 1. Question ONE is compulsory

2. Solve any THREE out of remaining questions

3. Draw neat and clean diagrams

4. Assume suitable data if required.

- Q. 1. A. Justify that JFET can be used as a Voltage Variable Resistor 5
B. With neat diagram explain any one application of Zero-Crossing Detector 5
C. With neat block diagram explain how PLL can be used to generate large number of frequencies from a single reference frequency. 5
D. Explain with suitable example what do you understand by signal multiplexing? 5
- Q. 2. A. Derive an expression for trans-conductance for JFET. 10
B. List down various parameters of Opamp along with their typical values for IC741. Also explain what the significance of CMRR and Slew Rate is? 10
- Q. 3. A. Explain how operational amplifier can be used for taking average of three signals. 5
B. Explain fly wheel effect in Class C amplifier. 5
C. Explain Nyquist criteria. 5
D. Determine the magnitude of g_m for a JFET with $I_{DSS} = 8 \text{ mA}$ and $V_p = -4 \text{ V}$ at dc bias points $V_{GS} = -0.5 \text{ V}$ and also at $V_{GS} = -2.5 \text{ V}$. 5
- Q. 4. A. Explain generation of SSB using phase shift method. 10
B. Explain the use of PLL as FM detector. 10
- Q. 5. A. Explain super heterodyne receiver in detail along with the waveforms at each stage. 10
B. Explain the concept of amplitude modulation. 10
- Q. 6. A. Write short note on generation of FM by Armstrong method. 5
B. Mention important specifications of ADC and DAC required for communication. 5
C. Explain the necessity and significance of modulation in communication. 5
D. Compare n-channel and p-channel JFET with respect to their device features and voltage-current characteristics. 5

FW-Con. 10510-16.