

EXTC

Analog Electronics II

QP Code : 4887

(3 Hours)

[Total Marks : 80]

N.B (1) Question Nos. 1 is compulsory.

(2) Attempt any three questions from the remaining five questions.

(3) Figure to the right indicates full marks.

(4) Assume suitable data whenever necessary but justify the same.


- 1 (a) Compare clipper and clamper circuit. [5]  
 (b) Explain Barkhausen criteria for sustained oscillations. [5]  
 (c) Compare Depletion and Enhancement type MOSFET. [5]  
 (d) Transistor is a current controlled device while FET is a voltage controlled device. Justify. [5]

Q2 (a) Define Stability factor. Derive the equation for Stability factor. State which biasing technique is more stable. Justify your answer. [10]

- (b) For a NPN transistor in CE mode voltage divider bias configuration determine  $V_C$  and  $V_B$ . Given  $V_{CC} = +20V$ ,  $V_{EE} = -20V$ ,  $R_1 = 8.2K\Omega$ ,  $R_2 = 2.2K\Omega$ ,  $R_C = 2.7K\Omega$ ,  $R_E = 1.8 K\Omega$ ,  $C_1=C_2= 10\mu F$  and  $\beta = 120$ . [10]

Q3 (a) Derive the equations for  $A_v$ ,  $A_i$ ,  $R_i$  and  $R_o$  for a NPN transistor in CE mode voltage divider bias configuration with  $R_E$  unbypassed. [10]

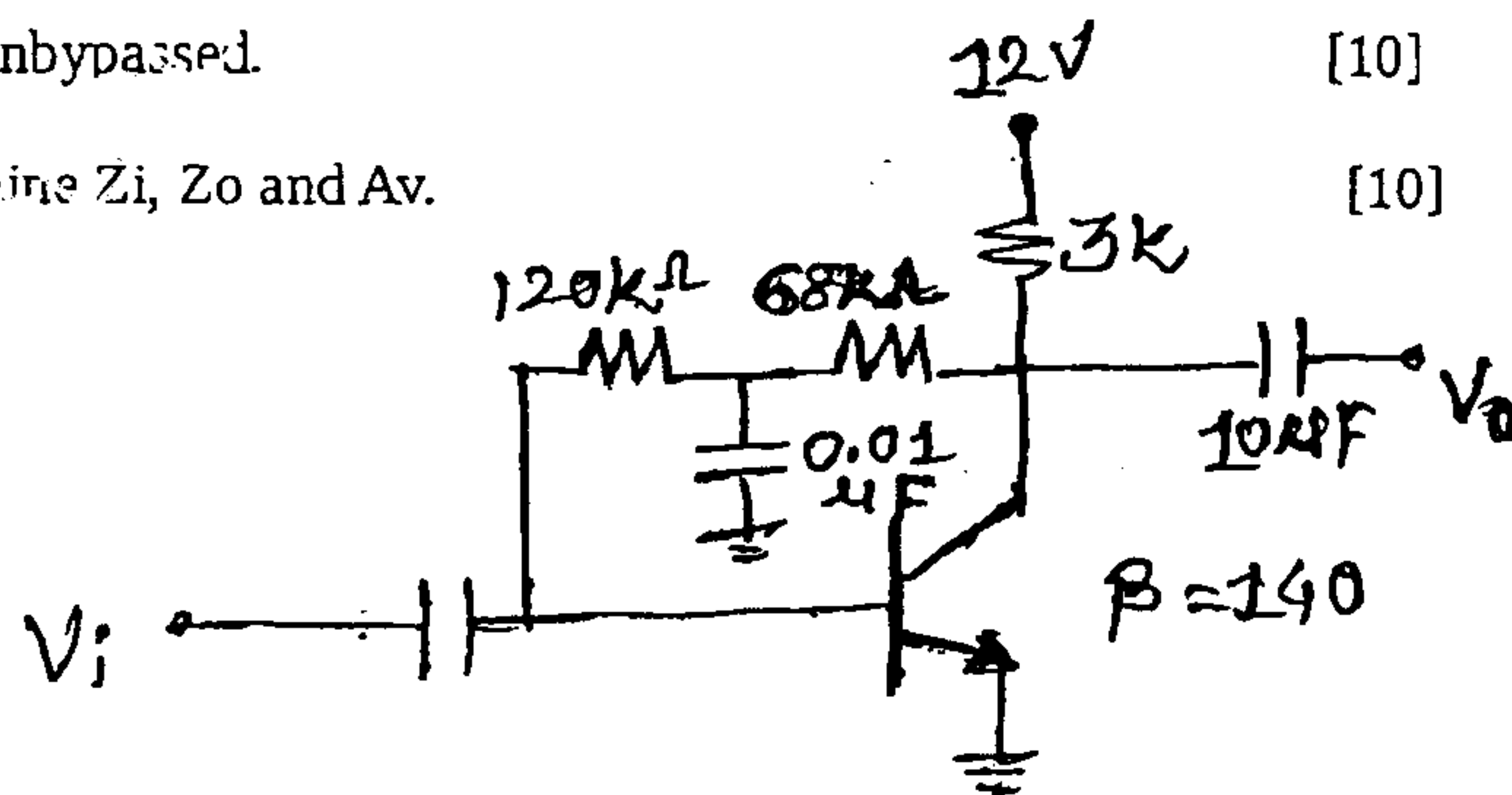- (b) For the network given below determine  $Z_i$ ,  $Z_o$  and  $A_v$ . [10]



Q4 (a) Explain the basic operation and characteristics of n-channel enhancement type MOSFET. [10]

- (b) Draw a neat circuit diagram of Wien bridge oscillator and derive an expression for its output frequency. [10]


JP-Con. 8919-15.

PT-0


(2)

QP Code : 4887

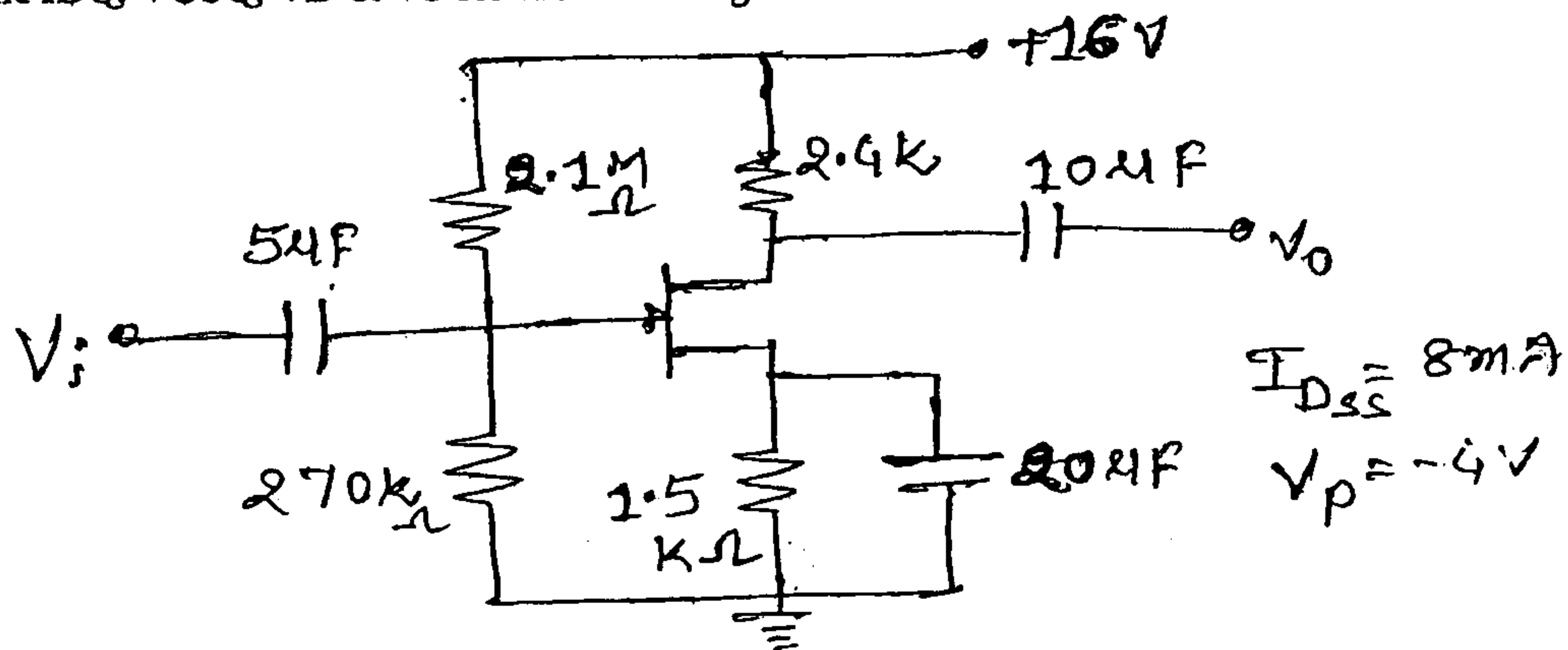Q5.) a) Determine  $I_{DQ}$ ,  $V_{GSQ}$ ,  $V_D$  &  $V_S$  for the network given below: [10]



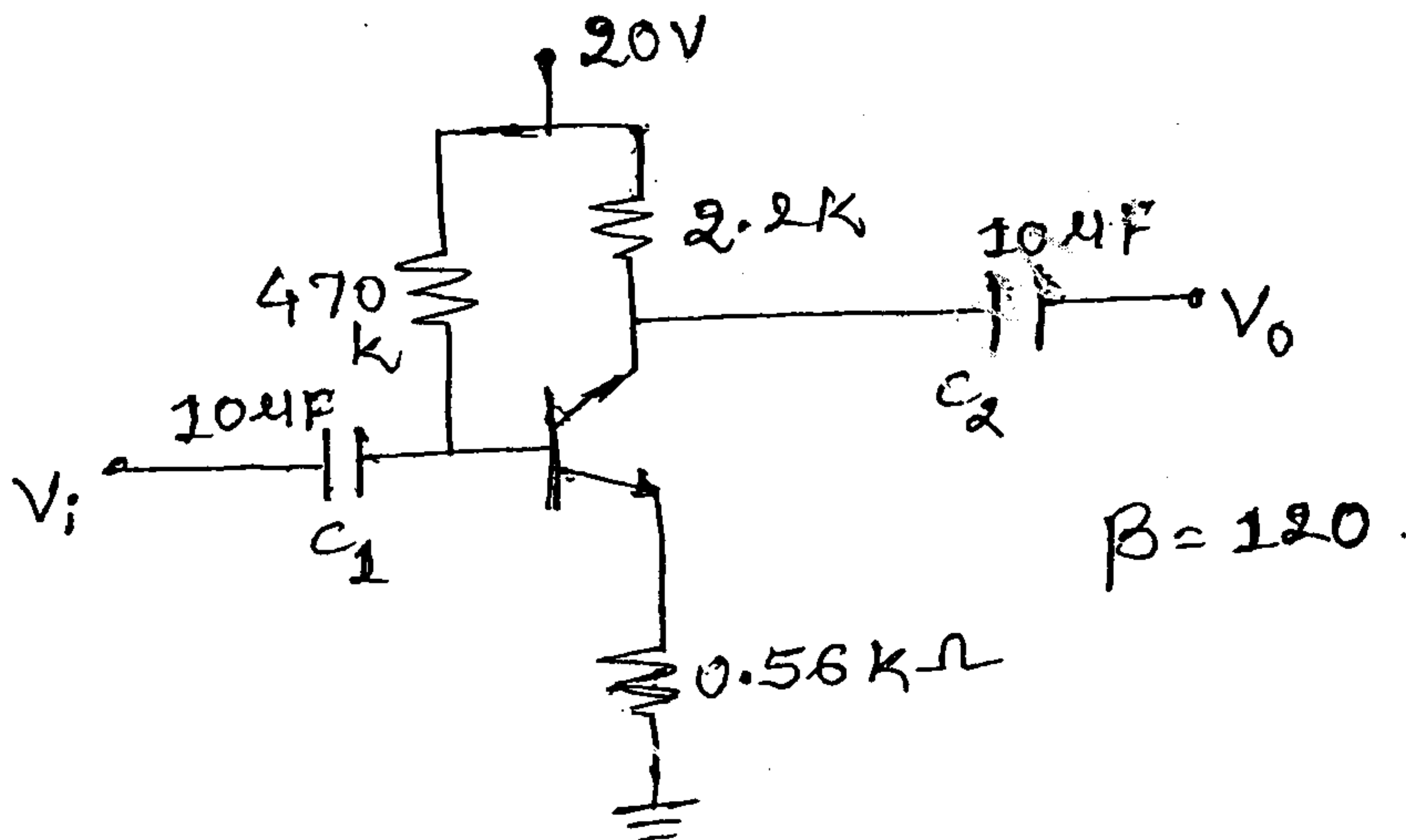b) Determine  $Z_i$ ,  $Z_o$  &  $A_v$  for the circuit given below. [10]



Q6. Write short note on any Four:- [20]

- i) Biasing of JFET for Zero temperature drift.
- ii) Energy band diagram of MOS capacitor.
- iii) Small signal equivalent circuit of CC amplifier.
- iv) Crystal oscillator
- v) DC load line & significance of Q point.

JP-Con. 8919-15.