
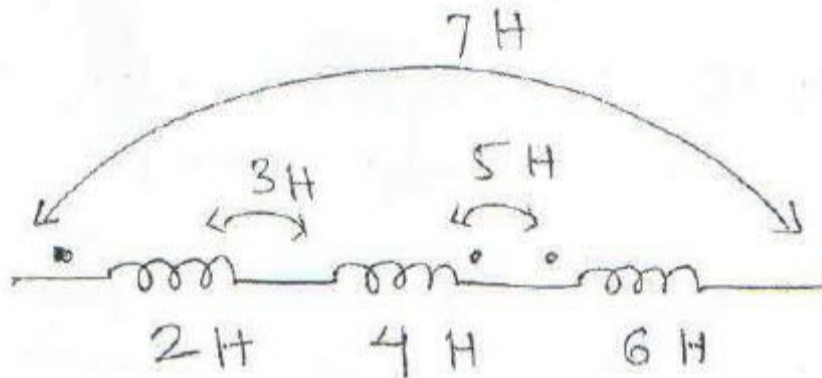


- N. B. :** (1) Question No. 1 is compulsory.  
 (2) Solve any **three** questions out of remaining **five** questions.  
 (3) **Figures** to the **right** indicate **full** marks.  
 (4) Use Smith Chart for transmission line problem.

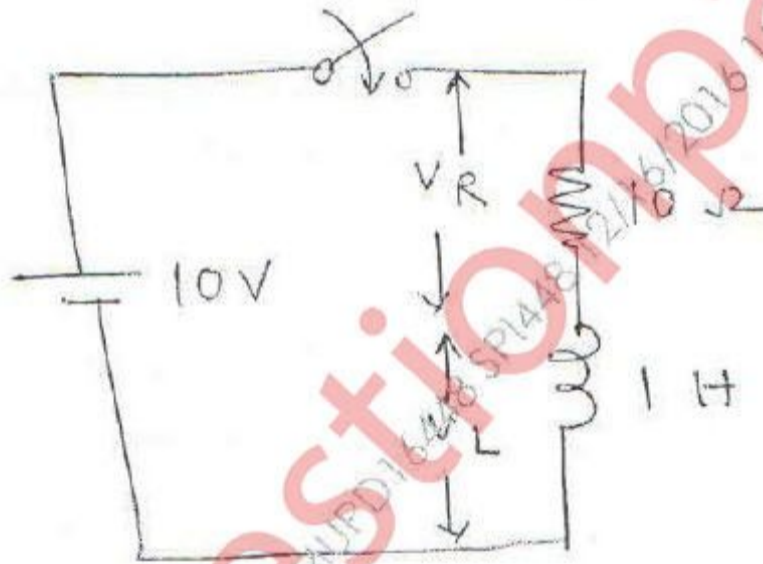
1. (a) Find the equivalent inductance of the network shown.




- (b) A series R-L circuit is shown in fig. has a constant voltage  $V$  applied at  $t = 0$ . At what time does  $V_R = V_L$



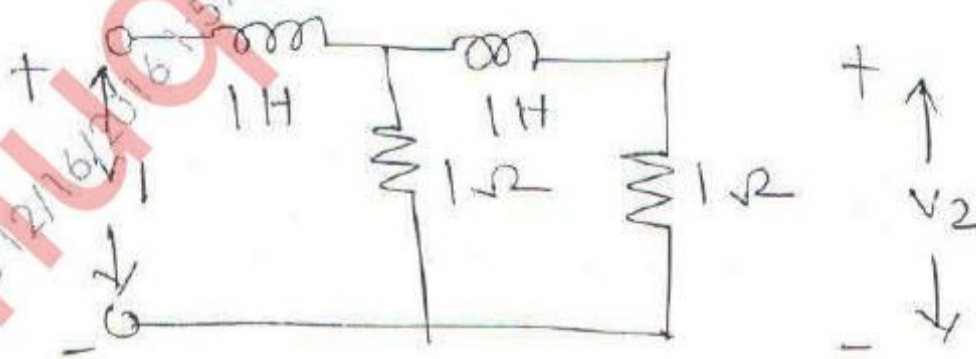
- (c) For the network shown plot poles and zeros of the transfer impedance function.



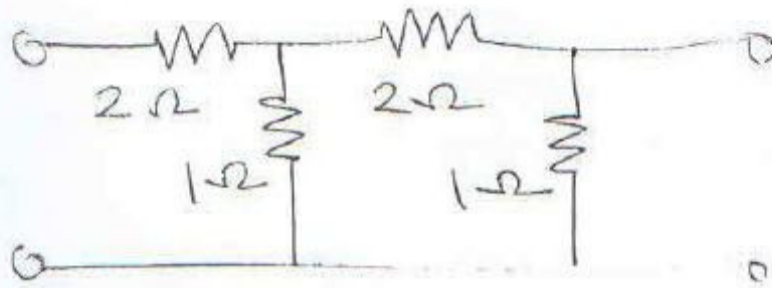(d) Determine h parameters of the network given.




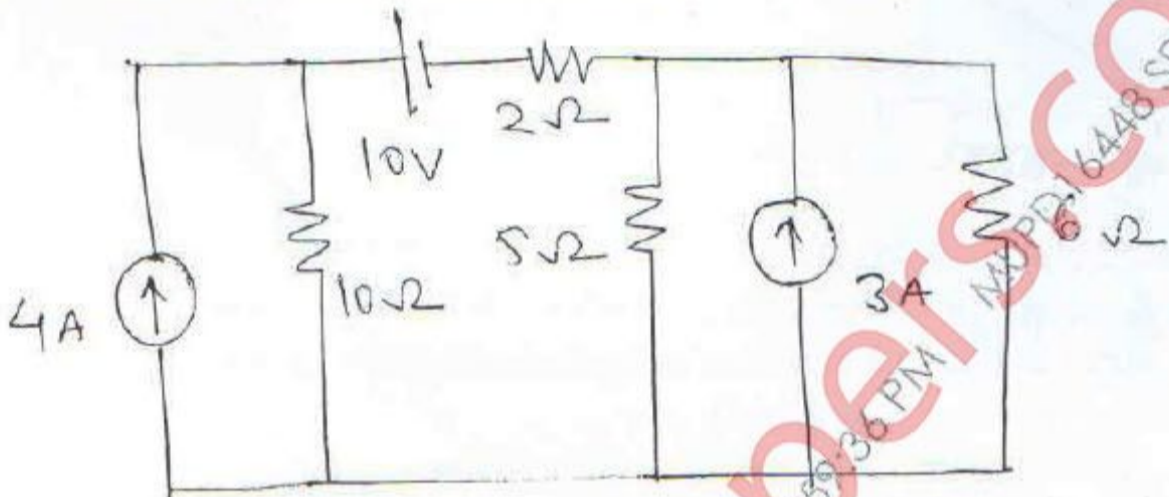2. (a) Find the current through  $6\Omega$  resistor in given circuit.



10

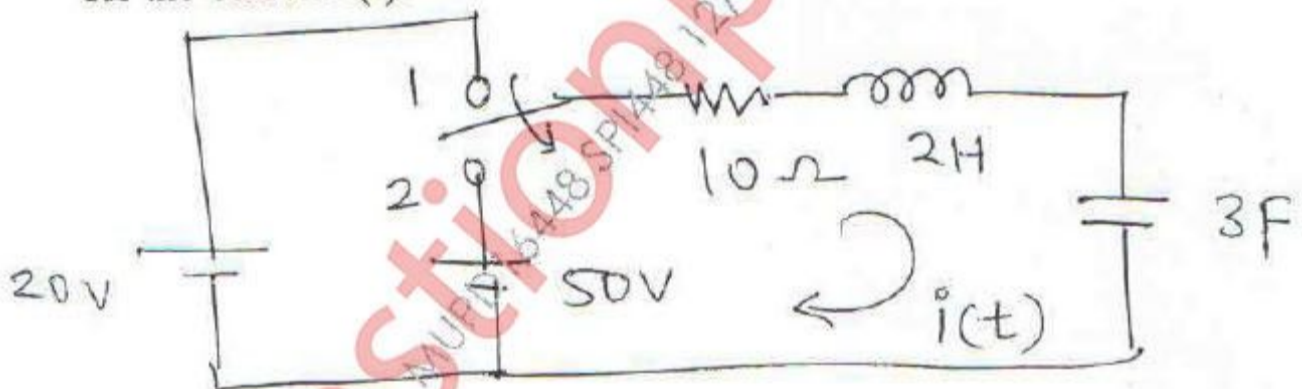(b) In the network shown switch is moved from position 1 to position 2. The switch is at position 1 for long time. Determine the expression for the current  $i(t)$ .



5

3. (a) Test whether  $F(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$  is a positive real function.

(b) Check whether the following polynomials are Hurwitz or not. Use continued fraction method.

(i)  $P(s) = s^7 + 2s^6 + 2s^5 + s^4 + 4s^3 + 8s^2 + 8s + 4$

(ii)  $P(s) = s^5 + s^3 + s$

(c) Realise caur forms of the following LC impedance function.


$$Z(s) = \frac{10s^4 + 12s^2 + 1}{2s^3 + 2s}$$

[ TURN OVER



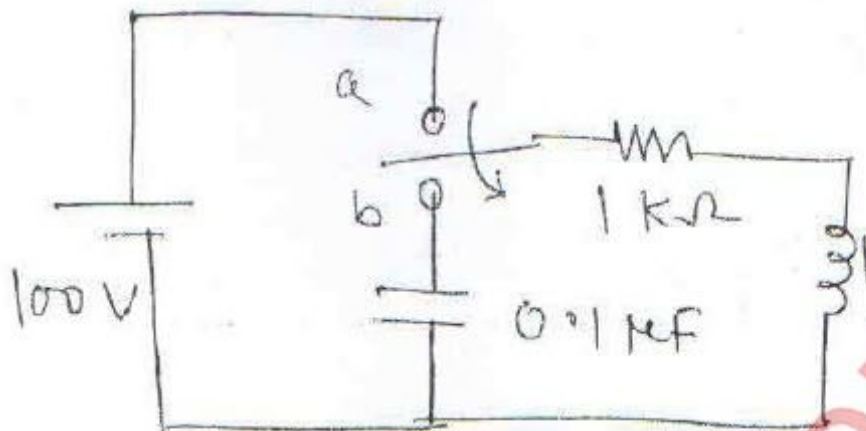
4. (a) In the network given the switch is changed from position a to b at 10

$t = 0$ . Find out  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$



- (b) The values of primary constants of an open wire line per km are  $R = 10\Omega$ ,  $L = 3.5 \text{ mH}$ ,  $C = 0.008 \mu\text{F}$  and  $G = 0.7 \mu\text{mho}$ . For a signal frequency of 1 KHz. Calculate  $z_0$ ,  $\gamma$ ,  $\alpha$ ,  $\beta$ ,  $\lambda$  and  $V_p$ . 10

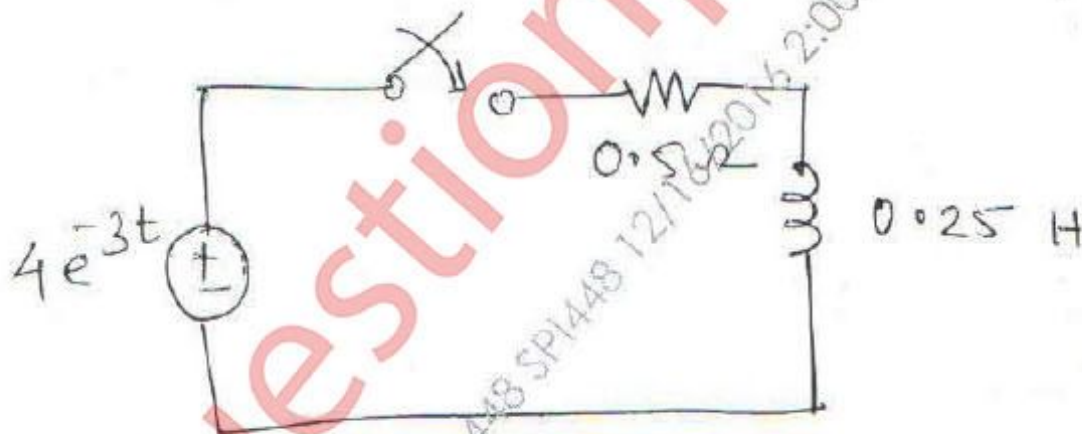5. (a) Find the expression for  $i(t)$ . 10





- (b) Design an  $m$ -derived  $\text{T}$  section high pass filter with a cut off frequency of 2 KHz. Design impedance of  $700\Omega$  and  $m = 0.6$ . 5

- (c) The char. impedance of a high frequency line is  $100\Omega$ . It is terminated in an impedance of  $100 + j100\Omega$ . Using Smith chart find the impedance 5

at  $\frac{1}{8}$  th wavelength away from the load end.

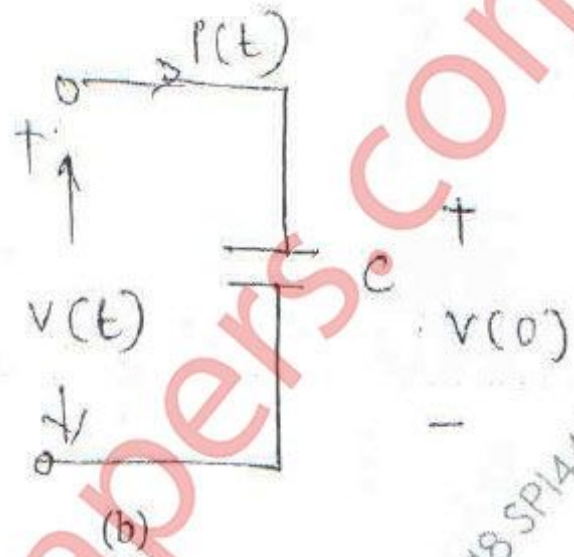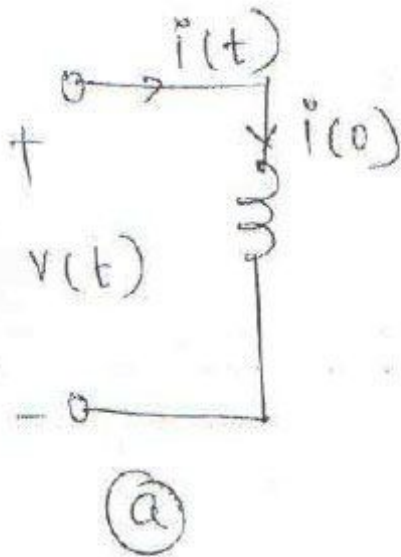6. (a) Draw and explain transformed network in s domain for given circuits. 5  
Use current and voltage equation.



- (b) A series RLC circuit has a quality factor of 5 at 50 rad/sec. The current flowing through the circuit at resonance is 10A and the supply voltage is 100V. Find the circuit constants. 5

- (c) For the given network determine  $\frac{v_2}{v_1}$  and  $\frac{i_2}{i_1}$  10

