

Digital Circuit & Design


(3 hours)

Total Marks :80

N.B.:

1. Question No. 1 is compulsory.
2. Attempt any 3 Questions from the remaining 5 Questions
3. Assume suitable data, wherever necessary

Q. No	Solve any four	Marks
Q 1.(a)	Write a truth table of half adder and write a VHDL code for half adder	5
Q 1.(b)	Explain advantages of JTAG architecture	5
Q 1.(c)	Explain advantages and drawback of synchronous counter.	5
Q 1.(d)	Explain the following terms: 1.Noise margin 2. Noise immunity 3. Propagation delay with reference to digital ICs	5
Q 1.(e)	Differentiate between multiplexer and demultiplexer	5
Q2.(a)	Design a Meal type sequence detector to detect three or more consecutive 1's in a string of bits coming through an input line.	10
Q 2.(b)	What are universal gates? Why are they called so? Implement XOR and XNOR function using all NAND gates.	10
Q 3.(a)		10

 

Analyze the sequential state machine shown in figure and obtain state diagram for the same

- | | | |
|---------|--|----|
| Q 3.(b) | Obtain excitation table for JK flip flop and convert JK flip flop to T flip flop. | 10 |
| Q 4.(a) | Draw a circuit diagram of 2 input TTL NAND gate and Explain the interfacing of TTL and CMOS. | 10 |

- Q4.(b) Design a MOD10 asynchronous counter using T flip flop 10
- Q5(a) Design a combinational circuit using a suitable PAL considering the following Boolean expressions. Use a PAL with four inputs and four outputs and three wide AND OR structure. 10
- $W(a,b,c,d) = \sum m(2,12,13)$
 $X(a,b,c,d) = \sum m(7,8,9,10,11,12,13,14,15)$
- Q5(b) Design 4 bit Johnson counter using J-K flip flop. Explain its working using waveform 10
- Q6(a) Write short notes on 20
1. Stuck at zero and stuck at 1 fault.
 2. Entity declaration and architecture declaration.
 3. FPGA architecture
 4. State reduction and state assignment.