


QP Code : NP-18678

(3 Hours)

[Total Marks : 80

- N.B. :** (1) Question No. 1 is compulsory.
 (2) Solve any **three** from remaining 5 questions.
 (3) Draw **neat** diagrams wherever **necessary**.

 1. (A) Implement the following function using NOR gates only. (after reduction using K map) 10
 $F = \pi M (1,2,4,7,11,13) . d (9,15)$
- (B) Design a MOD 6 asynchronous counter and explain glitch problem. 10
2. (A) Analyze the clocked synchronous machine given below. Write excitation equations, excitation/transition table and state /output table (Use state names A - D for Q1-Q2=00-11). Also draw the state diagram. 10



- (B) Design a 1 digit BCD adder using IC 7483 and explain the operation for $(0111)_{BCD} + (1001)_{BCD}$. 10
3. (A) Write a VHDL code for 8:1 Multiplexer with active low enable input. 10
- (B) Design a mealy sequence detector to detect a sequence ---1101---using D flip-flops and logic gates. 10
4. (A) Design a circuit with optimum utilization of PLA to implement the following functions 10
 $F1 = \sum m (1, 2, 3, 6, 9, 11)$
 $F2 = \sum m (0, 1, 6, 8, 9)$
 $F3 = \sum m (2, 3, 8, 9, 11)$
- (B) Implement following function using 4:1 line MUX and NAND gates. 10
 $F (A, B, C, D) = \sum m (1, 2, 6, 7, 10, 12, 13)$
5. (A) Design a 8 bit binary up counter using MSI counter IC 74163, draw a circuit diagram and explain working. 10
- (B) Eliminate redundant states and draw reduced state diagram. 10

PS	NS		O/P Y
	X = 0	X = 1	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

6. Write short notes on (Any THREE): 20
 1. XC 4000 FPGA Architecture
 2. Stuck at '0' and stuck at '1' fault
 3. Master Slave JK flip flop
 4. 2 input TTL NAND gate

-----S-----