

Sem- IV / CBGS / Mech / I.E / Nov-2016

28-12-16

Industrial Electronics

QP Code : 555700

( 3 Hours)

| Total Marks : 80



- N.B. :**
- (1) Question No. 1 is compulsory.
  - (2) Attempt any three questions out of remaining questions.
  - (3) Figures to the right indicate full marks.
  - (4) Assume suitable data if necessary.

1. Solve **any five** :-

20

- a) Draw characteristics of SCR, Triac, MOSFET and IGBT.
- b) Draw connection of an LED and a switch to MSP430.
- c) Explain basic principle of single phase inverter.
- d) Enlist characteristics of ideal op-amp.
- e) Give an example of analog circuit, digital circuit, combinational circuit and sequential logic circuit.
- f) Draw torque-speed characteristics of DC shunt motor and 3-phase induction motor.
- g) What do you understand by R-L and R-L-E load?

2. a) Explain in brief functional block diagram of MSP430.

7

b) Draw and explain block diagram of closed loop speed control of DC motor. Also state need of inner current loop.

7

c) Draw and explain any one application circuit of Triac-Diac.

6

3. a) Explain IC 555 as monostable multivibrator.

7

b) Explain frequency control scheme of 3-phase induction motor with the help of block diagram.

7

c) Write a short note on :- Turn-off of SCR.

6

4. a) Draw the circuit diagram of differentiator and integrator? Write the output equation of each.

7

b) Enlist triggering methods of SCR and explain any one gate triggering method of SCR.

7

c) What do you understand by a Digital circuit? Elaborate following terms regarding digital circuits :-

6

(i) logic level (ii) noise immunity (iii) propagation delay

(iv) power dissipation (v) fan out.

5. a) Elaborate: - Accuracy, Resolution and least significant bit regarding 10-bit ADC.

7

b) Write a short note on 'selection of motor and power rating for a pump'.

7

c) Explain asymmetrical semi controlled converter with R load and derive equation of output voltage.

6

6. a) Compare - BLDC motor, DC motor and induction motor.

7

b) Compare- Microprocessor and Microcontroller.

7

c) Compare- TTL and CMOS technology.

6