

Sem-V ETRX (CBGS) 17/5/16.

Design with linear Integrated
Circuit

QP Code : 31088

(3 Hours)

[Total Marks : 80

- N. B. : (1) Question No. 1 is compulsory.
(2) Solve any **three** out of remaining questions.
(3) Assume suitable data if necessary.

1. (a) Explain behaviour of op-amp in linear and saturation region with neat graphs. 20
(b) Explain non-inverting comparator with suitable example.
(c) State various methods to achieve analog to digital conversion.
(d) Explain 78XX series voltage regulator.
(e) Implement $y = 3v_a - 5v_b + 7v_c$ using op-amp, where y is output and v_a, v_b & v_c are inputs.
2. (a) Derive expression for voltage gain of inverting amplifier and hence design the same for voltage gain = 20. 10
(b) Design a 2nd order KRC low pass filter with a cutoff frequency $f_o = 1$ KHz and $Q = 5$. 10
3. (a) Draw the circuit diagram of an inverting type schmitt trigger circuit. Design such a circuit to meet $UTP = +2.5$ V & $LTP = -1$ V. Assume $\pm v_{sat} = \pm 12$ V, for an input of $8\sin\omega t$, plot the graph of v_o and v_{in} . 10
(b) Explain working of Wien bridge oscillator and hence design for $f_o = 5$ KHz. 10
4. (a) Explain R/2R ladder type DAC 10
(b) Design Mono stable multivibrator using IC 555 to generate output delay of 10 msec. 10
5. (a) Design voltage regulator using IC 723 for $V_o = 10$ V and $I_L = 200$ mA. 10
(b) Explain internal diagram of power amplifier LM 380 10
6. Write short notes on :- 20
 - (a) Sample and Hold circuit
 - (b) V-I converter
 - (c) Applications of IC 555
 - (d) Switching mode voltage regulator