

# 17213

**15116**

**3 Hours / 100 Marks**

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

- 1. Attempt any TEN of the following: **20****
- a) Define active components. Give one example.
  - b) Draw symbols of npn and pnp transistors.
  - c) State two applications of tunnel diode.
  - d) Define bandwidth of Amplifier.
  - e) Draw symbols of
    - (i) LED and
    - (ii) Tunnel diode
  - f) Give the applications of IC (any two)
  - g) State the need of filter.

P.T.O.

- h) Write two applications of oscillators.
- i) Define static resistance and dynamic resistance of diode.
- j) Give classification of  $IC_s$ .
- k) Draw circuit diagram of two stage RC coupled transistor amplifier.
- l) Draw symbols of fixed and variable capacitor.

**2. Attempt any FOUR of the following: 16**

- a) State the different types of Resistor. State any four specifications of Resistors.
- b) Explain operating principle of Varactor Diode.
- c) Explain operation of npn transistor with neat diagram.
- d) Compare BJT and JFET.
- e) Explain operation of P - N junction in forward biased condition.
- f) Draw and explain direct coupled amplifier with its frequency response.

**3. Attempt any FOUR of the following: 16**

- a) Draw and explain construction of LDR. Also explain its working principle.
- b) Explain the mechanism of zener breakdown in zener diode.
- c) Draw the construction of n - channel JFET and describe its working.
- d) Draw and explain circuit diagram of crystal oscillator.
- e) Define current gain and voltage gain. What is the need for multistage amplifiers?
- f) A transistor has  $\beta = 100$ . If its collector current ( $I_C$ ) = 50 mA, What is the value of  $I_B$  and  $I_E$  ?

- 4. Attempt any FOUR of the following:** **16**
- a) Draw and explain V - I characteristics of P - N junction diode.
  - b) Differentiate between half wave rectifier and centre tapped full wave rectifier. (four points)
  - c) Draw the circuit diagram of single stage CE amplifier. State functions of each component.
  - d) Draw circuit diagram of bridge rectifier along with its input and output waveforms.
  - e) Explain drain characteristics of JFET with neat diagram.
  - f) Define drain resistance, transconductance, amplification factor and input resistance.
- 5. Attempt any FOUR of the following:** **16**
- a) Explain the operating principle of LED. State any two applications of LED.
  - b) Explain the working of centre tapped full wave rectifier with neat diagram and also draw its input and output waveform.
  - c) Explain the working of zener diode as voltage regulator.
  - d) Draw the circuit of astable multivibrator using transistor. State its two applications.
  - e) Draw and explain V - I characteristics of schotkky diode.
  - f) Draw and explain transformer coupled amplifier with its frequency response.

**6. Attempt any FOUR of the following:****16**

- a) Differentiate between P - N junction diode and zener diode.  
(Any four points)
- b) Draw block diagram of regulated power supply. Draw output voltage waveforms at each block.
- c) Draw circuit diagram of voltage divider biasing circuit and state its two advantages.
- d) State and explain Barkhausen's criteria for oscillator.
- e) Explain the working principle and MOSFET with a suitable diagram.
- f) An ac supply of 230 V is applied to half wave rectifier circuit through transformer of turns ratio 2:1.

Calculate:

- (i) DC output voltage and
  - (ii) PIV of a diode.
-

17213

**15116**

**3 Hours / 100 Marks**

---