

21415

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--


- Instructions :** (1) All Questions are *compulsory*.  
(2) Illustrate your answers with neat sketches wherever necessary.  
(3) Figures to the right indicate full marks.  
(4) Assume suitable data, if necessary.

**Marks**

**1. Attempt any TEN :**

**20**

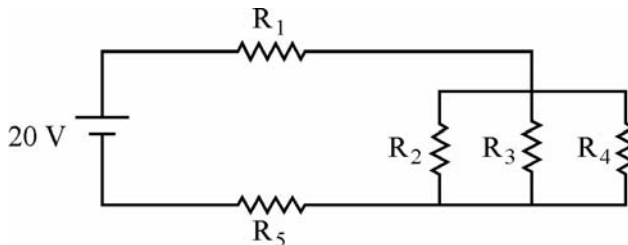- (a) Define Ferromagnetic materials. Draw B-H curve.
- (b) State two functions of slug-tuned inductor and write the expression of self inductance.
- (c) State the classification of capacitors.
- (d) State the need of rectifiers and filter.
- (e) Draw the circuit diagram of bridge rectifier and draw its output waveform.
- (f) Draw the ideal current source and practical current source.
- (g) State Kirchoff's Law (KCL, KVL)
- (h) Find the current flowing through  $R_1$  in following circuit :



$$R_1 = 100 \Omega, R_2 = 500 \Omega, R_3 = 750 \Omega, R_4 = 1000 \Omega, R_5 = 50 \Omega$$

- (i) Write two applications of P-N junction diode and zener diode.
- (j) Draw the symbol of
  - (1) Zener diode
  - (2) Schottky diode
  - (3) LED
  - (4) Tunnel diode
- (k) What is the meaning of linear and non-linear wave-shaping circuit ?
- (l) Draw RC integrator and differentiator.

**P.T.O.**

**2. Attempt any FOUR :****16**


- Describe the working of LDR with neat sketch and list applications of it.
- Compare linear and logarithmic potentiometers. (any four points)
- Draw the construction diagram of electrolytic capacitor and write the materials used for different parts.
- Write four specifications of capacitor. Write the range of values for any one type of capacitor.
- Draw the construction diagram of iron core inductor and write the working of it.
- Draw and describe the P-N junction diode characteristics.

**3. Attempt any FOUR :****16**

- List four specifications of zener diode or P-N junction diode.
- Draw the characteristics of tunnel diode and write two applications of it.
- Explain the working principle of Schottky diode with neat sketch.
- Describe the operating principle of LASER diode with diagram.
- Draw the circuit diagram of shunt capacitor filter along with full wave rectifier. Draw the waveform of full wave rectifier output and shunt capacitor filter output.
- Write the function of C and L in  $\pi$  filter and write two advantages of  $\pi$  filter over other filters.


**4. Attempt any FOUR :****16**

- Define :
  - PIV
  - TUF
  - Ripple factor
  - Efficiency of rectifier
- Explain the colour coding using colour-band system in capacitor with an example.
- The input AC power to HW rectifier is 140 W and DC power output is 60 W. Calculate the efficiency of rectification.
- Compare HW and FW (CT type) rectifier on the basis of :
  - PIV
  - Efficiency
  - Ripple Frequency
  - Necessity of transformer
- Compare P-N junction diode with zener diode.
- Calculate the value R in the following circuit to get maximum forward current of 100 mA
  - when diode is Si-diode
  - when diode is Ge-diode

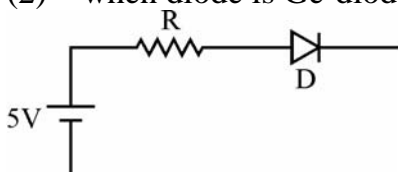


5. Attempt any FOUR :

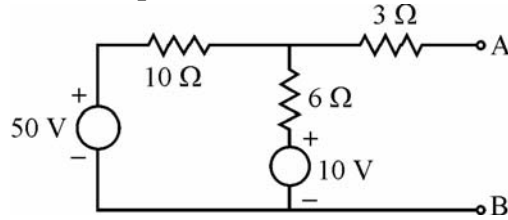
- (a) Draw the positive clamper circuit and explain its working.
- (b) Draw the clipper circuit using series and shunt diode
- (c) Find the Thevenin's equivalent circuit for the circuit shown in fig.



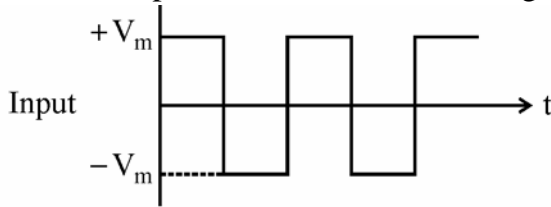
- (d) Compare RC integrator and differentiator.
- (e) Draw the output waveform for following circuits when input is




Circuits (1)

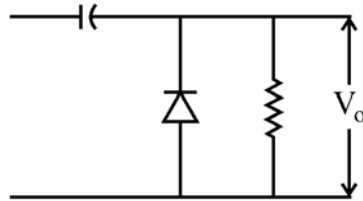


(2)

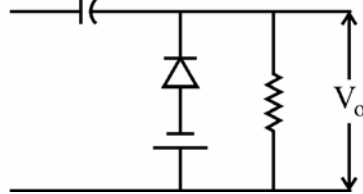

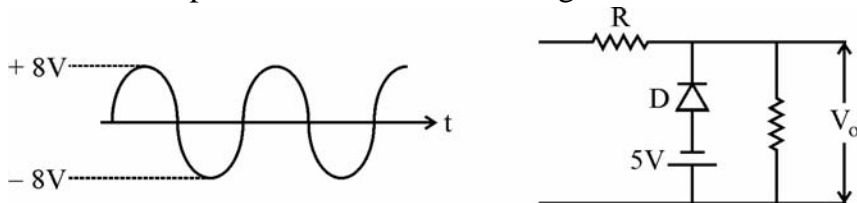- (f) (i) Draw the output waveform for following circuit :




- (ii) Draw the circuit for following input and output :

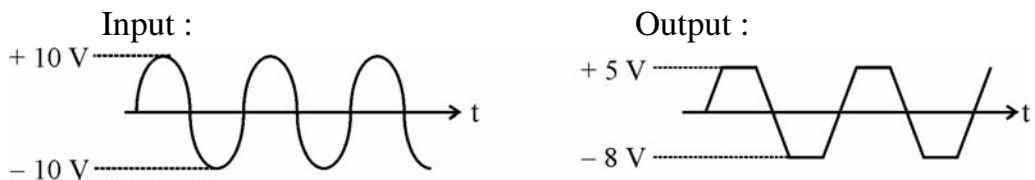


6. Attempt any FOUR :

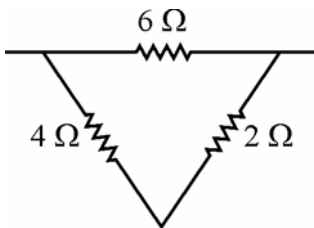- (a) Compare clipper and clamper.
- (b) State the condition for RC differentiator. Draw the output waveform of RC integrator for square wave input.
- (c) Compare :
  - (1) Active network and passive network.
  - (2) Linear network and non-linear network.
- (d) Convert the delta network into equivalent star network.



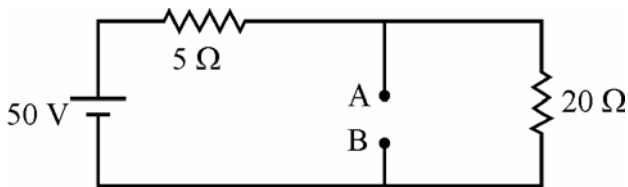- (e) Find the Norton's current through AB



- (f) (1) State the maximum power transfer theorem.
- (2) For the circuit shown in fig, determine the value of load resistance when load resistance draws maximum power. Also find the value of the maximum power.

