

17215

15162

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**


**1. Attempt any TEN :**

**20**

- (a) Define ferromagnetic and ferrimagnetic material. Give one example of each.
- (b) Draw B-H curve for hard and soft magnetic material.
- (c) List four dielectric materials used for capacitors.
- (d) State the necessity of rectifier and filter circuits.
- (e) List advantages of bridge rectifier.
- (f) Define Kirchoff's voltage law.

**P.T.O.**

- (g) State value of internal resistance of ideal current and ideal voltage source.
- (h) Find current through resistor  $R_3$ .

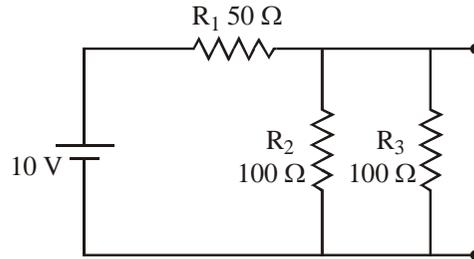

(Fig. 1)

- (i) Draw symbol and state one application of zener diode and LED.
- (j) List applications of Schottky diode and Laser diode.
- (k) Write two applications of clipper and two applications of clamper.
- (l) Define clipper. Draw circuit of negative shunt clipper.

## 2. Attempt any FOUR :

16

- (a) Give classification of resistors. List any four materials used for manufacturing of resistor.
- (b) With the help of neat diagram, describe working of LDR.
- (c) Describe working of variable air gang capacitor.
- (d) Using four band colour code, find resistance value for
- Brown Red Red Silver
  - Yellow Violet Orange Gold
- (e) Write difference between iron core inductor and ferrite core inductor.
- (f) State and explain operating principle of photodiode.

**3. Attempt any FOUR :****16**

- (a) Draw and describe construction of LED.
- (b) Draw and describe V-I characteristics of P-N junction diode.
- (c) Define dynamic resistance of diode. State, how it is calculated using forward characteristics of diode.
- (d) Compare zener diode and P-N junction diode.
- (e) Draw circuit and describe working of full wave rectifier using centre tapped transformer.
- (f) Define given parameters and state their values for bridge rectifier.
  - (i) Ripple factor
  - (ii) PIV of diode

**4. Attempt any FOUR :****16**

- (a) Draw circuit of capacitor filter with bridge rectifier. Draw input and output waveforms.
- (b) Explain the working principle of electrolytic capacitor.
- (c) Compare inductor filter and capacitor filter.
- (d) A bridge rectifier is delivering dc power to load resistance of  $1\text{ k}\Omega$ . AC voltage of  $230\text{ V}$  is given to rectifier through transformer with turn ratio  $10 : 1$ . Find
  - (i) Peak output current  $I_m$
  - (ii) DC output current  $I_{dc}$(Consider diode and transformer as ideal)


**P.T.O.**

- (e) Draw the characteristics of tunnel diode, showing operating regions. State two applications of tunnel diode.
- (f) State operating principle of LED. Write material names used to manufacture LED.

5. Attempt any FOUR :

16

- (a) Draw and describe working of positive clamper.
- (b) Compare linear and non-linear waveshaping networks.
- (c) For given circuit (Fig. 2). Find

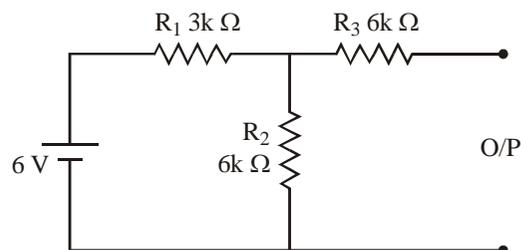

(Fig. 2)

- (i) Open circuit output voltage and output current.
- (ii) Short circuit output voltage and output current.
- (d) With the help of circuit diagram and waveforms, explain working of RC differentiator.


- (e) If three resistors of  $10\ \Omega$  each are connected in delta connection. Convert it into star connection. Draw circuit diagram for both.
- (f) State (i) Norton's theorem.  
(ii) Super-position theorem

6. Attempt any FOUR :


16

- (a) Draw RC integrator circuit. Write expression for  $V_o$ . Draw input and output waveforms for square-wave input.
- (b) Draw output waveforms for following circuits :

(Consider diodes as Si diodes)

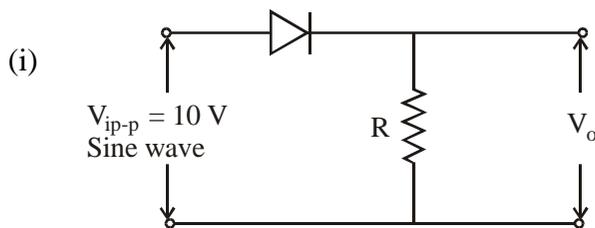


(Fig. 3)

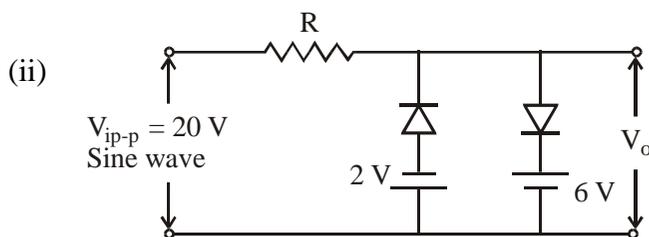


(Fig. 4)

- (c) State Thevenin's theorem. Find Thevenin's resistance  $R_{TH}$  for given circuit.

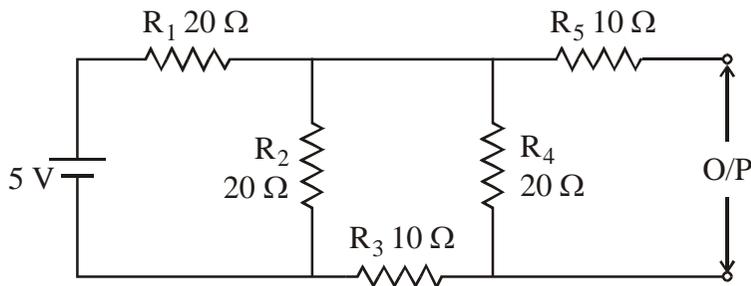


(Fig. 5)

- (d) Find current through resistance  $R_4$  using super-position theorem.

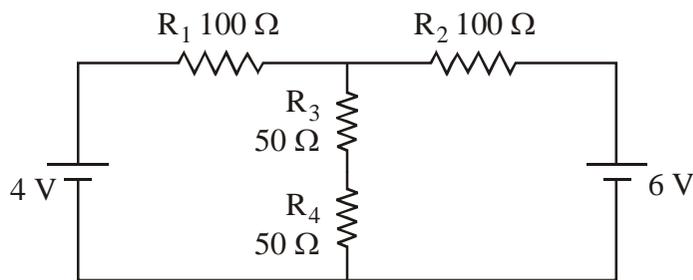

(Fig. 6)


- (e) For the given circuit,

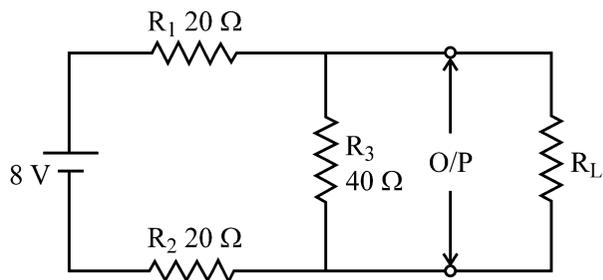

(Fig. 7)

- find (i) Load resistance  $R_L$  to which maximum power will be transferred.  
 (ii) Maximum power transferred to load  $R_L$ .

- (f) Using Maxwell's loop current method, write equations for Loop-A and Loop-B

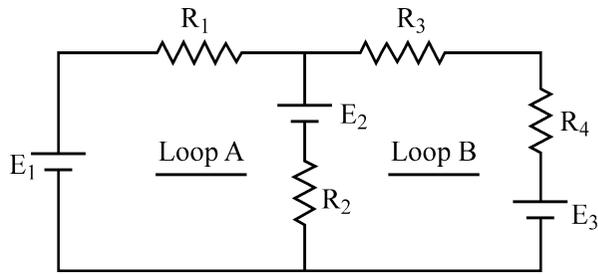

(Fig. 8)

---

