

17319

14115

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* – (1) All Questions are *Compulsory*.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data, if necessary.
- (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
- (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. a) Attempt any **SIX** of the following : **12**
- i) List various transistor biasing method.
 - ii) Define α of Transistor.
 - iii) State the need of cascade amplifier.
 - iv) Define intrinsic stand off ratio for UJT.
 - v) Define operating principle of tuned circuit.
 - vi) List the types of power amplifiers.
 - vii) State the effect of V_{GS} on channel conductivity of N-channel JFET.
 - viii) Draw the circuit diagram of bootstrap time base generator.

P.T.O.

- b) **Attempt any TWO of the following :** **8**
- i) Draw the circuit diagram of CB configuration, and Draw output characteristic with different regions.
 - ii) Draw circuit diagram of fixed voltage bias-method and describe its working.
 - iii) Draw functional block diagram of IC 723 and write the function of IC 723.
2. **Attempt any FOUR of the following :** **16**
- a) State the need for biasing in transistor, List any two method.
 - b) Draw the circuit diagram of voltage divider bias method and describe its working.
 - c) Draw the construction of N-channel JFET and explain its working.
 - d) What is amplifier ? Give the classification of amplifier.
 - e) State effect of negative feed back on voltage gain, bandwidth, I/P impedance, O/P impedance.
 - f) Draw the block diagram of regulated power supply. Write the function of each block.
3. **Attempt any FOUR of the following :** **16**
- a) Compare CB, CE, CC of BJT with reference to following point.
 - i) I/P impedance
 - ii) Current gain
 - iii) O/P impedance
 - iv) Voltage gain
 - b) Explain how JFET acts as voltage controlled device ?
 - c) State the Barkhausen criterion for the generation of sustained oscillations and draw block diagram of an oscillator.
 - d) Draw frequency response of direct coupled amplifier. Discuss its advantages and disadvantages.
 - e) State the working principle of 79XX series voltage regulator with diagram.
 - f) Draw the circuit diagram of series transistor voltage regulator and describe its operation.

- 4. Attempt any FOUR of the following :** **16**
- a) Draw the symbol and construction of N-Channel JFET.
 - b) Draw the circuit diagram of double tuned amplifier and sketch the frequency response.
 - c) Compare BJT and JFET with reference to following point.
 - i) Symbol
 - ii) Transfer characteristic
 - iii) I/P impedance
 - iv) Application
 - d) Draw circuit diagram of complementary symmetry class B push pull power amplifier and describe its operations.
 - e) Compare small signal amplifier and power amplifier for two points.
 - f) Draw the V-I characteristics of U.J.T. and label it.
- 5. Attempt any FOUR of the following :** **16**
- a) In CE configuration if $\beta = 99$ leakage current $I_{CEO} = 50 \mu A$ if base current is 0.5 mA, Determine I_C and I_E .
 - b) Compare RC oscillator and crystal oscillator with reference to following point.
 - i) Frequency stability
 - ii) Example
 - iii) Application
 - iv) Frequency formula
 - c) Draw circuit diagram of single stage class A amplifier and describe its working.
 - d) List four applications of FETs.
 - e) Draw the circuit diagram of crystal oscillator, and give the basic principle of piezoelectric crystal.
 - f) Describe the working of zener diode as a voltage regulator.

- 6. Attempt any FOUR of the following :** **16**
- a) Derive the relation between α and β of transistor.
 - b) Describe the working principle of UJT as a relaxation oscillator with neat circuit diagram.
 - c) Compare negative and positive feed back effect with respect to
 - i) Gain
 - ii) BW
 - iii) Z_i
 - iv) Z_o
 - d) Compare single tuned and double tuned circuit from following point.
 - i) Selectivity
 - ii) Q-factor
 - iii) Bandwidth
 - iv) Response of Gain Vs frequency
 - e) State need of voltage regulator. Define load and line regulation.
 - f) Draw miller sweep generator and give any two applications.
-