

17318

16172

3 Hours / 100 Marks

Seat No.

|  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.
  - (8) Use of steam tables, logarithmic, Mollier's chart is permitted.

**Marks**

**1. Attempt any TEN of the following :**

**20**

- (a) Define (i) Form factor (ii) Peak factor.
- (b) Draw the waveforms of voltage and current of pure capacitive circuit.
- (c) Define phase sequence in 3-phase ac supply.
- (d) Define the bandwidth of a series resonant circuit and give expression of the same.
- (e) Draw Torque – Slip characteristics of induction motor.
- (f) State specification and two applications of Isolation transformer.
- (g) State Fleming's Right Hand Rule.
- (h) State an electric motor suitable for table fan.
- (i) Give classification of types of wires used in electrical installation.
- (j) Give any two differences between AC and DC quantity.

- (k) List the factors considered for selection of intermediate frequency transformer.
- (l) Draw neat constructional sketch of auto transformer.
- (m) List the speed control methods of 3-phase induction motors.
- (n) Alternating current is given by  $i = 28.28 \sin (2\pi 50 \times t)$  Find R.M.S. value of current.

**2. Attempt any FOUR of the following :**

**16**

- (a) Equations for current and voltage in a circuit are given by :

$$V = V_m \sin \omega t$$

$$i = I_m \sin (\omega t + 90^\circ)$$

State what type of circuit is it ? Draw waveforms of voltage, current and power for the circuit.

- (b) Explain why 1- $\phi$  I.M. (induction motors) do not have starting torque.
- (c) Explain the necessity of earthing.
- (d) Define and explain the meaning of Q-factor and give expression for Q-factor in RLC series circuit.
- (e) A delta connected balanced load has impedance of  $(3 + j 4) \Omega$  connected to a 230 V, 3 $\phi$ , 50 Hz A.C. supply. Calculate value of line and phase currents line and phase voltages, power consumed by each impedance and total power consumed.
- (f) Draw Torque-Speed characteristics of 3 $\phi$  induction motor and explain.

## 3. Attempt any FOUR of the following :


16

- Differentiate between core type and shell type transformer.
- Explain the working principle of a single phase transformer.
- State the necessity of starter in case of three phase induction motor.
- Draw the schematic representation of split phase induction motor. State its applications.
- Draw a 3-phase star connected supply system and state the relation between  $V_{ph}$  and  $V_L$ ,  $I_{ph}$  and  $I_L$ . State an expression to determine power in the circuit.
- Explain the phenomenon of resonance in R-L-C series circuit.
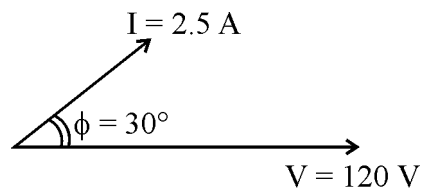
## 4. Attempt any FOUR of the following :

16

- State four advantages of polyphase circuits over single phase circuits.
- For a phasor diagram shown in Fig., find (i) Impedance (ii) Power factor (iii) Total power (iv) Values of components connected in series. Assume  $f = 50$  Hz.



- Compare statically induced emf to dynamically induced emf.
- State different types of powers in Electrical Circuit. Draw power triangle and write units for each power.
- Explain the concept of lagging and leading of I or V by waveform and mathematical equation in AC circuit.
- Compare universal motor with servomotor on the basis of (1) Construction (2) Size (3) Cost (4) Torque developed (5) Application.

P.T.O.

**5. Attempt any FOUR of the following :****16**

- (a) What are the different ways of interconnection of phases in a 3-phase system ?  
Why is it required ?
- (b) Define efficiency and % voltage regulation of a transformer.
- (c) State and explain Faraday's laws of electromagnetic induction and its two applications in electrical engineering.
- (d) Why transformer rating is given in terms of kVA and not in kW ?
- (e) Explain the working of A.C. servo motor with a neat diagram.
- (f) For a R-C circuit
  - (i) Draw circuit diagram
  - (ii) Write voltage and current equations
  - (iii) Draw vector diagram
  - (iv) Draw impedance triangle

**6. Attempt any FOUR of the following :****16**

- (a) Compare squirrel cage induction motor and slipring induction motor.
  - (b) State and explain Fleming's Right hand rule.
  - (c) Define synchronous speed, slip and rotor frequency.
  - (d) Explain working of 3 ph induction motor.
  - (e) What is power factor ? State its significance.
  - (f) Explain the necessity of earthing and state any four safety precautions while working with electrical system.
-