

17318

11718

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :** (1) All Questions are *compulsory*.  
(2) Illustrate your answers with neat sketches wherever necessary.  
(3) Assume suitable data, if necessary.  
(4) Use of Non-programmable Electronic Pocket Calculator is permissible.  
(5) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

**1. Attempt any TEN of the following :**


**20**

- (a) Define form factor and peak factor.
- (b) Write any two difference points between a.c. and d.c. supply.
- (c) Draw the voltage waveform of three phase a.c. supply for 0 to  $2\pi$ .
- (d) State the concept of phase sequence.
- (e) State the Faraday's law of electromagnetic induction.
- (f) State Lenz's law.
- (g) Define transformation ratio and voltage ratio of transformer.
- (h) What is the main purpose of using isolation transformer in electronic circuits ?
- (i) Mention any two methods to control speed of  $3\phi$  I.M.
- (j) Define synchronous speed and slip of  $3\phi$  I.M.
- (k) Write down any two applications of servo motor.
- (l) State specialty of universal motor.
- (m) State the importance of ELCB in circuit.
- (n) List any four tools used for safety in workshop.

## 2. Attempt any FOUR :

16

- (a)  $V = 200 \sin \left( 314 t + \frac{\pi}{3} \right)$ . Determine :
- (i) Frequency (ii)  $V_{\text{rms}}$
- (iii)  $V_{\text{avg}}$  (iv) Phase angle
- (b) Draw the waveform and phasor diagram for current and voltage when a.c. flows through a purely capacitive circuit. Also write equation for voltage and current.
- (c) A coil of resistance  $10 \Omega$  and inductance  $0.01 \text{ H}$  are connected in series with  $100 \mu\text{F}$  capacitor across  $230 \text{ V}$ ,  $50 \text{ Hz}$  a.c. supply. Find :
- (i)  $X_L$  (ii)  $X_C$
- (iii)  $Z$  (iv)  $I$
- (d) Draw the phasor diagram of R-L-C series circuit when
- (i)  $X_L > X_C$  (ii)  $X_L = X_C$  (iii)  $X_L < X_C$
- (e) A series R-L circuit takes a current of  $2 \text{ A}$  when connected to  $200 \text{ V}$ ,  $50 \text{ Hz}$  a.c. supply and consumes  $300 \text{ watts}$ . Calculate resistance, inductance, impedance and power factor.
- (f) For below shown phasor diagram of R-L-C series circuit find (i) Impedance (ii) Power factor (iii) Power consumed (iv) Nature of circuit

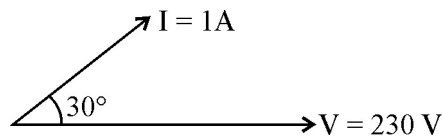

**3. Attempt any FOUR :****16**

- (a) Draw the power triangle and define active power, reactive power and apparent power.
- (b) Give the significance of power factor. Write down the power factor for purely inductive, capacitive and resistive circuit.
- (c) State the condition for resonance. Write about the value of current during series resonance. Show the graphical representation of current in series resonance circuit.
- (d) Define resonant frequency and Q-factor. Give relation of each.
- (e) List the advantages of 3 $\phi$  supply over single phase (any four).
- (f) Give relation between line and phase current, line and phase voltage for 3 $\phi$  balanced (i) Star connected and (ii) Delta connected load.

**4. Attempt any FOUR :****16**

- (a) Three impedances of  $(4 + 3j)$  ohms each are connected in star to a 3 $\phi$ , 440 V, 50 Hz balance a.c. supply. Calculate line voltage, phase voltages, line current phase current, power factor and power.
- (b) Draw delta connected 3 $\phi$  load and show line and phase voltages and current on it.
- (c) Explain self induced emf, mutually induced emf and dynamically induced emf.
- (d) State Fleming's right hand rule and write down formula for energy stored in magnetic field.
- (e) Define regulation and efficiency of transformer. Which transformer will be said to be a quality transformer one with regulation 2% or the other with regulation 4% ?
- (f) Write down one application of each transformer :
  - (i) Audio freq.
  - (ii) Radio freq.
  - (iii) Intermediate freq.
  - (iv) Pulse transformer

**P.T.O.**

**5. Attempt any FOUR :****16**

- (a) A 1.5 kVA, 230/110 V, 50 Hz single phase transformer has 80 turns on secondary winding. Calculate number of primary turns full load primary and secondary currents.
- (b) State the emf equation of a single phase transformer. Write meaning of each term.
- (c) Can auto transformer be used as step up and step down transformer ? If yes, show the circuits.
- (d) Explain the working principle of 3 $\phi$  I.M.
- (e) Draw the torque-speed characteristics of 3 $\phi$  I.M. Explain about the nature.
- (f) Define synchronous speed. Write down the formulas for slip, slip speed, rotor frequency.

**6. Attempt any FOUR :****16**

- (a) Explain the speed control method of 3  $\phi$  I.M. using variable frequency drive using thyristor.
  - (b) Write down the constructional difference between squirrel cage and slip ring 3 $\phi$  I.M.
  - (c) Explain the working principle of stepper motor. Mention its types. Write any two applications.
  - (d) State the working principle of a.c. servo motor and draw its torque speed characteristics.
  - (e) Give the necessity of earthing. State the range of voltage between earth and neutral of healthy wiring.
  - (f) Write advantages of MCCB over fuse (any four).
-