



17318

14115

3 Hours/100 Marks

Seat No.

--	--	--	--	--	--	--	--

Instructions : (1) **All** questions are **compulsory**.

(2) Answer **each** next main question on a **new** page.

(3) Illustrate your answers with **neat** sketches **wherever** necessary.

(4) Figures to the **right** indicate **full** marks.

(5) Assume suitable data, if **necessary**.

(6) Use of Non-programmable Electronic Pocket Calculator is **permissible**.

(7) Mobile Phone, Pager and any other Electronic Communication devices are **not permissible** in Examination Hall.

MARKS

1. Attempt **any ten** :

20

- a) Write definition and formula of power factor.
- b) State any two disadvantages of low power factor in supply system.
- c) Write the formula of 3-phase power and relation between line voltage and phase voltage in 3 ϕ star connected system.
- d) Define resonance in series R-L-C circuit and write the formula of resonance frequency.
- e) Define and write formula of
 - I) Slip
 - II) Synchronous speed
- f) State the E.M.F. equation of transformer and write meaning of each term in the formula.
- g) State the Faraday's laws of electromegnetic induction.
- h) List any two applications of
 - I) Stepper motor
 - II) Servo motor

P.T.O.



- i) Define :
- I) Minimum fusing current
 - II) Fusing factor.
- j) Write the full form of following
- I) ELCB
 - II) MCB
 - III) MCCB
 - IV) HRC (Fuse)
- k) Define :
- I) % regulation
 - II) % efficiency of transformer and write formula for it.
- l) What will happen if transformer is connected to DC supply ?
- m) How the direction of 3 phase induction motor can be reversed ?
- n) Draw only a circuit diagram and phasor diagram of an ac R-L series circuit.

2. Attempt **any four** :

16

- a) What are effects of change in frequency on inductive and capacitive reactance ? Also write the formula for X_L and X_C .
- b) Why single phase motors are not self starting ? How it is made self starting ?
- c) What is earthing ? Draw only schematic diagram of pipe earthing.
- d) Define :
- I) Cycle
 - II) Frequency
 - III) Time period
 - IV) Amplitude of AC voltage
- e) Three impedances each of 3-ohm resistance and 5-ohm-reactance in series are connected in star across 50 Hz, 440 volt line voltage. Find
- I) Impedance
 - II) Phase current
 - III) Power factor
 - IV) Total power
- f) Compare 3 ϕ slip ring motor and squirrel cage motor based on following point
- I) Construction and cost
 - II) Starting torque
 - III) Power factor and efficiency
 - IV) Methods of starting.



3. Attempt **any four** :

16

- a) Why the core of a transformer is laminated ? Write only the names of losses in transformer and method to reduce the losses.
- b) Write any two applications of
 - I) Pulse transformer
 - II) Auto transformer
 - III) Audio transformer
 - IV) Intermediate frequency transformer.
- c) List out the speed control methods for 3 phase induction motor. Explain any one with neat sketches.
- d) Draw neat sketch and write working principle of shaded pole single phase motor.
- e) Compare single phase and three phase system on the basis of following point
 - I) Output
 - II) Efficiency
 - III) Cost
 - IV) Power factor
- f) For a given equation of voltage and current in a circuit $v = V_m \sin \omega t$, $i = I_m \sin (\omega t + 90^\circ)$.
State what type of circuit is it. Draw wave form of voltage, current and power in the circuit.

4. Attempt **any four** :

16

- a) What is the principle of 3 phase E.M.F. generation ? Draw its wave form.
- b) An alternating voltage is given as $e = 250 \sin 314.16 t$ than find
 - I) R.M.S. value
 - II) Maximum value
 - III) Frequency
 - IV) Value of voltage at $t = 05 \text{ ms}$.
- c) Define dynamically induced EMF and explain principle of mutually induced EMF.
- d) Define alternating current and write any three advantages of AC over DC voltage.
- e) What is auto transformer ? Write any three applications of auto transformer.
- f) Draw only circuit diagram of a single phase capacitor start induction run motor. What is the use of centrifugal switch ? And write any one application of it.

5. Attempt **any four** :

- a) What is meant by a 3 phase balanced and unbalanced load ?
- b) Define the following term as related to AC supplies
 - I) Form factor
 - II) Peak factor
 - III) Q-factor
 - IV) Impedance
- c) Write any four factors upon which an inductance of a coil depends.
- d) Write the property of ideal transformer and also write the formula for transformation ratio.
- e) Explain with neat sketch working principle of universal motor.
- f) Compare series and parallel resonance circuits (any four points).

6. Attempt **any four** :

- a) Explain in brief the construction and working principle of 3-phase induction motor.
 - b) Write the symbol and unit of following :
 - I) Magnetic flux density
 - II) Magnetic field strength
 - III) Reluctance
 - IV) Co-efficient of self inductance
 - c) Draw neat sketch and write working principle of direct online starter for small squirrel cage induction motor.
 - d) Write any four applications of
 - I) 3-phase slipring induction motor
 - II) Squirrel cage induction motor
 - e) Define active, reactive and apparent power in AC circuit. Write the unit of each power and draw power triangle for an inductive load.
 - f) Write any two general precautions while using electrical energy. Define lagging power factor and leading power factor.
-