



# 17302

16117

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) *All questions are compulsory.*
  - (2) *Illustrate your answers with neat sketches wherever necessary.*
  - (3) *Figures to the right indicate full marks.*
  - (4) *Assume suitable data, if necessary.*
  - (5) *Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.*

**Marks**

1. a) Attempt **any six** :

12

- i) What is semiconductor ? Give two examples.
- ii) What is rectifier ? How are they classified ?
- iii) Draw the symbol of NPN and PNP transistor.
- iv) List any four applications of op-amp.
- v) Draw the logical symbol of 4 : 1 multiplexer.
- vi) Define :
  - a) Active and
  - b) Passive transducer
- vii) Define mechatronics.
- viii) State any four advantages of mechatronics.

b) Attempt **any two** :

8

- i) With the help of neat diagram explain the working of half wave rectifier.
- ii) List and explain any four features of ideal op-amp.
- iii) Draw the block diagram of FMS and explain the function of each block.

2. Attempt **any four** :

(4×4=16)

- a) What is the need of biasing circuit ? List the various types of biasing circuit for transistors.
- b) With the help of neat sketch explain how BJT is used as switch.
- c) Draw the circuit diagram of inverting amplifier. Calculate  $R_F$  if gain is 10 and  $R_1 = 1k\Omega$ .
- d) Draw the diagram of astable multivibrator and explain its working.
- e) Define oscillator. State Barkhausen criteria for oscillation.
- f) Draw the half adder circuit. Also write its truth table.

**P.T.O.**

**3. Attempt any four:****(4×4=16)**

- a) Draw the circuit diagram of RC coupled amplifier. Explain its working.
- b) Draw the logical symbol and write truth table for
  - a) AND gate
  - b) NOR gate.
- c) Compare microprocessor and microcontroller (any four points).
- d) What is decoder and encoder? State their applications (any two).
- e) With the help of suitable example explain the concept of primary and secondary transducer.
- f) Draw the functional block diagram of CMC and explain the function of each block.

**4. Attempt any four:****(4×4=16)**

- a) Draw the ladder diagram to verify the truth table of NOT gate and OR gate.
- b) Draw the circuit diagram of direct coupled amplifier. State its any two applications.
- c) Explain the criteria for the selection of PLC for an application.
- d) What is ADC and DAC state their application (any two)?
- e) Draw the block diagram of single channel data acquisition system. Explain the function of each block.
- f) Explain the working principle of
  - a) Photo diode
  - b) LDR.

**5. Attempt any four:****(4×4=16)**

- a) What is signal condition? Explain with the help of diagram AC signal conditioning.
- b) Explain any four criteria for selection of a transducer for an application.
- c) Draw the symbol and write any two applications of
  - a) UJT and
  - b) Zener Diode.
- d) What is opto coupler? How it is used as an isolator?
- e) Draw the construction of decade counter using T-flip flop.
- f) Compare intrinsic and extrinsic semi conductor.

**6. Attempt any four:****(4×4=16)**

- a) What do you mean by load regulation and line regulation?
  - b) Draw the block diagram of regulated power supply. State its two applications.
  - c) What is crystal oscillator? State its any four applications.
  - d) Draw the block diagram of SR flip flop. Write its truth table.
  - e) What is PLC? Explain the function of input module of PLC.
  - f) Draw 4-bit asynchronous counter circuit.
-