

11718

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. (A) Attempt any SIX of the following : 12
- (a) Draw the symbols of (i) SCR (ii) DIAC
 - (b) State advantages of power transistor (any two)
 - (c) Define holding and latching current.
 - (d) Define chopper. State its types.
 - (e) List different turn-on methods of SCR.
 - (f) State the applications of inverter.
 - (g) State the use of free wheeling diode in controlled rectifiers.
 - (h) Draw the circuit diagram of fan speed regulator using TRIAC.
- (B) Attempt any TWO : 8
- (a) Compare controlled and uncontrolled rectifiers. (any four points)
 - (b) Draw the circuit diagram and waveforms of step up chopper using MOSFET.
 - (c) Draw the circuit diagram of light dimmer using DIAC and TRIAC and sketch the input-output waveforms.

2. Attempt any FOUR :**16**

- (a) Draw the circuit diagram input-output waveforms and explain the working of single phase half wave controlled rectifier with R load.
- (b) Draw and explain the circuit diagram of series inverter with waveforms.
- (c) Draw the circuit diagram of emergency lighting system using SCR and describe its working.
- (d) Draw and explain the VI characteristics of DIAC.
- (e) Explain SCR triggering using UJT with neat circuit diagram.
- (f) Compare step up and step down chopper. (any four points)

3. Attempt any FOUR :**16**

- (a) Compare SCR & TRIAC. (any four points)
- (b) Draw the neat circuit diagram and waveforms of single phase centre tapped full wave controlled rectifier with RL load.
- (c) Draw and explain the VI characteristics of power transistor.
- (d) Draw and explain the VI characteristics of VJT.
- (e) Draw the circuit diagram of single phase fully controlled bridge rectifier with R load. Draw the waveforms of input and output voltage.
- (f) Describe the need of polyphase rectifier.

4. Attempt any FOUR :**16**

- (a) Draw the circuit diagram and waveforms of step down chopper and explain it.
- (b) Draw and explain the VI characteristics of SCR.
- (c) Describe the working of DC flasher circuit using SCR with neat diagram.
- (d) Draw the neat block diagram of gate triggering. State the advantages of gate triggering.
- (e) Draw the circuit diagram of temperature controller using SCR with neat circuit diagram.
- (f) Draw the circuit diagram of three phase half wave uncontrolled rectifier. Draw its input and output waveforms.

5. Attempt any FOUR :**16**

- (a) Draw and explain the battery charger using SCR.
- (b) Draw the construction of GTO & explain the working principle.
- (c) Describe the operation of pulse transformer used in triggering circuits.
- (d) Explain RC triggering circuit with neat circuit diagram & waveforms.
- (e) Draw the symbol & vertical structure of power transistor and explain.
- (f) Define firing angle and conduction angle. What is the effect of firing angle on average output voltage ?

P.T.O.

6. Attempt any FOUR :**16**

- (a) Draw and explain the diagram of electronic timer using SCR.
 - (b) Draw the circuit diagram of three phase controlled half wave rectifier with R load. Draw its input and output waveforms.
 - (c) Draw & explain the class C commutation with neat circuit diagram and waveforms.
 - (d) Draw and explain the two transistor analogy of SCR.
 - (e) Describe the construction of IGBT.
 - (f) Define commutation. List various types of commutation.
-