

17444

15162

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.

Marks

1. (A) Attempt any SIX :

2 × 6 = 12

- (a) Name any two triggering devices used for SCR.
- (b) List two features of IGBT.
- (c) Define (i) Latching current and (ii) Holding current.
- (d) List two applications of chopper.
- (e) Define commutation. What is the meaning of natural commutation ?
- (f) State the concept of chopper.
- (g) Define firing angle and conduction angle.
- (h) State any two applications of UPS.

(B) Attempt any TWO :

4 × 2 = 08

- (a) Compare controlled and uncontrolled rectifier (any four points).
- (b) Define inverter and give classification of inverter.
- (c) Draw the labelled circuit diagram of Electronic Timer using SCR.

2. Attempt any FOUR :

4 × 4 = 16

- (a) Draw the circuit diagram and input and output voltage waveforms of 3 ϕ half wave rectifier with resistive load.
- (b) Draw the circuit diagram of step-up chopper and state its operating principle.

P.T.O.

- (c) State the working of temperature controller circuit using SCR with neat diagram.
- (d) State the advantages and applications of GTO.
- (e) Describe the working of Class-B commutation with neat circuit diagram.
- (f) State different performance parameters of inverter and describe any two in details.

3. Attempt any FOUR :**4 × 4 = 16**

- (a) Draw V-I characteristics of DIAC. Is DIAC equally sensitive in both the directions ? Give two applications of DIAC.
- (b) Draw and explain single phase half wave controlled rectifier circuit with RL load.
- (c) Draw the two transistor model of SCR and explain it.
- (d) Compare power BJT, power MOSFET and IGBT (any four points).
- (e) Describe the effect of free wheeling diode in controlled rectifiers.
- (f) Draw the single phase full wave bridge type controlled rectifier. Draw the waveforms of input voltage, load voltage and voltage across SCR.

4. Attempt any FOUR :**4 × 4 = 16**

- (a) Define the following terms w.r.t. inverters :
 - (i) Harmonic factor of n^{th} harmonic
 - (ii) Total harmonic distortion
 - (iii) Distortion factor
 - (iv) Lowest order harmonics.
- (b) What is SMPS ? State types of SMPS. Sketch block diagram of SMPS and label it will.
- (c) Describe LASCR. Give its industrial applications.
- (d) List various forced commutation methods. Explain self commutation by resonating load.
- (e) With neat sketch, explain SCR based battery charger circuit. Which component avoid overcharging ?
- (f) State different advantages of MOSFET inverter.

5. Attempt any FOUR :**4 × 4 = 16**

- (a) Draw the neat circuit diagram of emergency lighting system using SCR and describe its working.
- (b) Draw V-I characteristics of PUT and describe the role of its operating regions.
- (c) What is the poly phase rectifier ? State its need.
- (d) Describe the operation of pulse transformer used in triggering circuits.
- (e) Draw labelled layer diagram of N-Channel IGBT. Draw its V-I characteristics.
- (f) Differentiate between single phase controlled half wave rectifier and single phase controlled full wave rectifier.

6. Attempt any FOUR :**4 × 4 = 16**

- (a) Sketch circuit diagram of low power DC flasher and state how flashing occurs.
 - (b) A single phase half wave rectifier is used to supply power to load impedance 10Ω from 230 V, 50 Hz A.C. supply at firing angle 30° . Calculate average load voltage.
 - (c) Compare natural and forced commutation.
 - (d) State one application each for
 - (i) SCR
 - (ii) PUT
 - (iii) TRIAC and
 - (iv) GTO
 - (e) Explain dv/dt turn on method of an SCR.
 - (f) State any two features of power MOSFET. Which makes it suitable for medium power applications ?
-

